

## **Electronics Fundamentals**

CIRCUITS, DEVICES, AND APPLICATIONS

**Eighth Edition** 

Thomas L. Floyd David M. Buchla



## **CONTENTS**

Application of Ohm's Law 124 Voltage Sources in Series 128

					1
Part	I DC Circuits 1		4–6 4–7	Kirchhoff's Voltage Law 131 Voltage Dividers 135	
	Quantities and Units	3	4-8	Power in Series Circuits 142	
1-1	Scientific and Engineering Notation 4		4–9 4–10	Voltage Measurements 144 Troubleshooting 148	
1-2	Units and Metric Prefixes 9		4-10	Application Assignment: Putting Your Kno	wledge
-3	Metric Unit Conversions 11			to Work 152	wiedge
-4	Measured Numbers 13			10 WOIR 102	
-5	Electrical Safety 16			p. II.I.d.	470
	50000 \$60000000 (#60000000 <b>#</b> 0) - 0.000		5	Parallel Circuits	170
2	Voltage, Current, and Resistance	24	5-1	Resistors in Parallel 171	
		Here a	5-2	Total Parallel Resistance 174	
-1 -2	Atoms 25		5-3 5-4	Voltage in a Parallel Circuit 179 Application of Ohm's Law 182	
3	Electrical Charge 28 Voltage 31		5-5	Application of Ohm's Law 182 Kirchhoff's Current Law 185	
4	Current 37		5-6	Current Dividers 189	
5	Resistance 40		5-7	Power in Parallel Circuits 193	
	The Electric Circuit 48		5-8	Troubleshooting 195	
	Basic Circuit Measurements 55			Application Assignment: Putting Your Kno	wledge
	Application Assignment: Putting Your Knowledge			to Work 200	
	to Work 62		6	Series-Parallel Circuits	219
3	Ohm's Law, Energy, and Power	75	6-1	Identifying Series-Parallel Relationships	220
1	Ohm's Law 76		6-2	Analysis of Series-Parallel Resistive Circui	
2	Application of Ohm's Law 80		6-3	Voltage Dividers with Resistive Loads 23	
-3	Energy and Power 85		6-4	Loading Effect of a Voltmeter 237	
-4	Power in an Electric Circuit 88		6-5	The Wheatstone Bridge 239	
-5	The Power Rating of Resistors 90		6-6	Thevenin's Theorem 244	
-6	Energy Conversion and Voltage Drop in a		6-7	The Maximum Power Transfer Theorem	252
	Resistance 93		6-8	The Superposition Theorem 254	
3–7 3–8	Power Supplies and Batteries 95		6–9	Troubleshooting 259	
-0	Introduction to Troubleshooting 98 Application Assignment: Putting Your Know to Work 101	ledge		Application Assignment: Putting Your Kno to Work 263	wiedge
			7	Magnetism and Electromagnetism	284
4	Series Circuits	115	7-1	The Magnetic Field 285	
-1	Resistors in Series 116		7-2	Electromagnetism 291	
-2	Total Series Resistance 118		7–3	Electromagnetic Devices 297	
-3	Current in a Series Circuit 122		7-4	Magnetic Hysteresis 303	
1-4	Application of Ohm's Law 124		7-5	Electromagnetic Induction 305	

7-6

DC Generators 310

7–7	DC Motors 314 Application Assignment: Putting Your Knowledge to Work 318		Inductors in AC Circuits 518 Inductor Applications 525 Application Assignment: Putting Your Knowledge to Work 527
Part	II AC Circuits 327	1	RL Circuits 537
8-1 8-2 8-3 8-4 8-5 8-6 8-7 8-8 8-9	Introduction to Alternating Current and Voltage 329  The Sinusoidal Waveform 330  Voltage and Current Values of Sine Waves 335  Angular Measurement of a Sine Wave 339  The Sine Wave Formula 343  Analysis of AC Circuits 347  Alternators (AC Generators) 351  AC Motors 355  Nonsinusoidal Waveforms 358  The Oscilloscope 365  Application Assignment: Putting Your Knowledge to Work 371	12-4 12-5 12-6	Circuits 539 Analysis of Series <i>RL</i> Circuits 541
9	Capacitors 388	B	RLC Circuits and Resonance 581
9-1 9-2 9-3 9-4 9-5 9-6 9-7	The Basic Capacitor 389 Types of Capacitors 395 Series Capacitors 401 Parallel Capacitors 405 Capacitors in DC Circuits 407 Capacitors in AC Circuits 415 Capacitor Applications 423 Application Assignment: Putting Your Knowledge to Work 428  RC Circuits 443	13-3 13-4 13-5 13-6	Impedance and Phase Angle of Series RLC Circuits 582 Analysis of Series RLC Circuits 583 Series Resonance 588 Series Resonant Filters 595 Parallel RLC Circuits 603 Parallel Resonance 608 Parallel Resonant Filters 616 Applications 622 Application Assignment: Putting Your Knowledge to Work 626
10-1	Sinusoidal Response of Series RC Circuits 444	14	Transformers 636
10-2 10-3 10-4 10-5 10-6 10-7 10-8 10-9	Impedance and Phase Angle of Series RC Circuits 445 Analysis of Series RC Circuits 447 Impedance and Phase Angle of Parallel RC Circuits 457 Analysis of Parallel RC Circuits 460 Analysis of Series-Parallel RC Circuits 464 Power in RC Circuits 469 Basic Applications 473 Troubleshooting 479 Application Assignment: Putting Your Knowledge to Work 484	14-1 14-2 14-3 14-4 14-5 14-6 14-7 14-8	Mutual Inductance 637 The Basic Transformer 638 Step-Up and Step-Down Transformers 642 Loading the Secondary 645 Reflected Load 648 Impedance Matching 650 Transformer Ratings and Characteristics 653 Tapped and Multiple-Winding Transformers 656 Troubleshooting 661 Application Assignment: Putting Your Knowledge to Work 663
<b>O</b>	Inductors 499	B	Time Response of Reactive Circuits 675
11-1 11-2 11-3 11-4	The Basic Inductor 500 Types of Inductors 505 Series and Parallel Inductors 506 Inductors in DC Circuits 508	15-1 15-2	The RC Integrator 676 Response of RC Integrators to a Single Pulse 677

15-3	Response of <i>RC</i> Integrators to Repetitive Pulses 682		Troubleshooting 870 Application Assignment: Putting Your Knowledge
15-4			to Work 873
15-5	Single Pulse 686 Response of <i>RC</i> Differentiators to Repetitive Pulses 691	19	Basic Op-Amp Circuits 88
15-6	Response of <i>RL</i> Integrators to Pulse Inputs 693	19-1	Comparators 886
15-7	Response of <i>RL</i> Differentiators to Pulse	19–2	Summing Amplifiers 889
15-8	Inputs 698 Applications 701	19-3 19-4	Integrators and Differentiators 893 Oscillators 899
15-9	Troubleshooting 704	19-5	Active Filters 905
	Application Assignment: Putting Your Knowledge	19–6	Voltage Regulators 913
	to Work 706		Application Assignment: Putting Your Knowledge to Work 921
Part	III Devices 717	20	Special-Purpose Op-Amp Circuits 93
_		20-1	Instrumentation Amplifiers 934
16	Diodes and Applications 719	20-2	Isolation Amplifiers 938
16-1	Introduction to Semiconductors 720	20–3	•
16-2	The Diode 726	20_4	(OTAs) 943 Active Diode Circuits 950
16-3	Diode Characteristics 731		Current Sources and Converters 956
16-4 16-5	Diode Rectifiers 735 Power Supplies 744		Application Assignment: Putting Your Knowledge
16-6	Special-Purpose Diodes 751		to Work 958
16-7	Troubleshooting 758		
	Application Assignment: Putting Your Knowledge	4	Measurement, Conversion, and Control 97
	to Work 765	21-1	Temperature Measurement 971
1	Total de la live de la companya de l	21–2	Strain, Pressure, and Flow Rate
W	Transistors and Applications 780	21-3	Measurements 980 Motion Measurement 985
17–1	DC Operation of Bipolar Junction Transistors	21-4	
17–2	(BJTs) 781 BJT Class A Amplifiers 785	21-5	graph water a 🚅 jugan - sawa 🚅 graph water graph a nahay gay a sawa
17-3	BJT Class B Amplifiers 798	21–6	Power-Control Circuits 996
17–4	The BJT as a Switch 804		Application Assignment: Putting Your Knowledge to Work 1000
17–5	DC Operations of Field-Effect Transistors		AND
17-6	(FETs) 806 FET Amplifiers 814	APPF	NDICES
17-7	Feedback Oscillators 819	-	
17-8	Troubleshooting 825	A	Table of Standard Resistor Values 1011
	Application Assignment: Putting Your Knowledge to Work 829	В	Capacitor Color Coding and Marking 1012
		C	Norton's Theorem and Millman's Theorem 1016
18	The Operational Amplifier 845	D	Field-Programmable Analog Arrays (FPAAs) 1021
18-1	Introduction to the Operational Amplifier 846	E	NI Multisim for Circuit Simulation 1030
18-2 18-3	The Differential Amplifier 848 Op-Amp Parameters 854		
18-4	Negative Feedback 860	Answe	ers to Odd-Numbered Problems 1035
18–5	Op-Amp Configurations with Negative	Glossa	агу 1048
19 6	Feedback 862 Op-Amp Resistances 867	Indov	1057
18-6	Op-Amp Resistances 867	muex	103/